

Experiment 9: Single Phase, Phase controlled Bi-directional AC to AC controller using TRIAC with R and R-L load

Introduction to the Experiment

This experiment is aimed to study the operation of Single Phase, Phase controlled Bidirectional AC to AC controller using TRIAC with R and R-L load by observing the output waveforms. The circuit is implemented in simulation as well as hardware and the performance is studied.

Learning outcomes:

Circuit Diagram:

Case I: with R Load

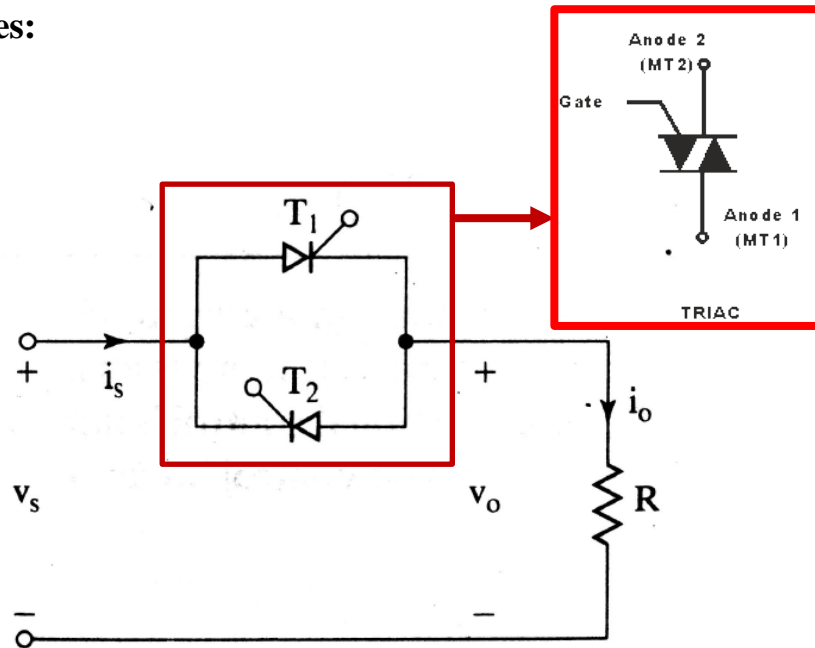


Figure 1 Circuit diagram with R load

Case II: With RL load


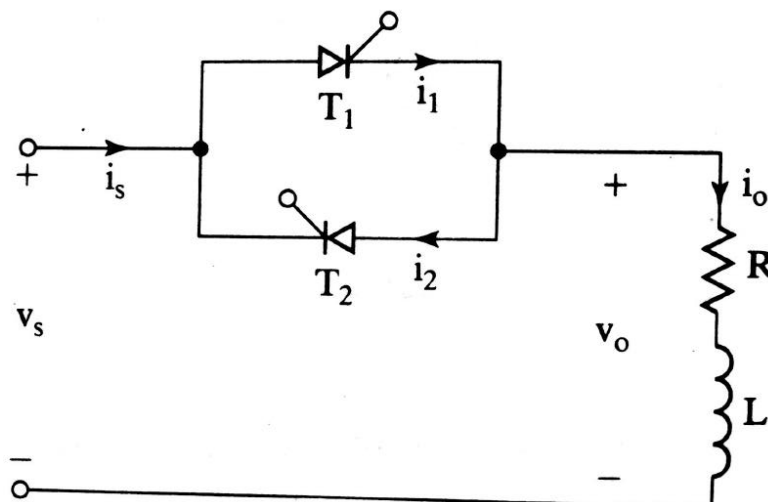


Figure 2 Circuit diagram with RL load

Theory:

AC to AC voltage converters operates on the AC mains essentially to regulate the output voltage. Portions of the supply sinusoidal appear at the load while the semiconductor switches block the remaining portions. They are called Phase Angle Controlled (PAC) AC-AC converters or AC-AC choppers. The TRIAC based converter may be considered as the basic topology. Being bi-directionally conducting devices, they act on both polarities of the applied voltage.

Waveforms for Case 1: R Load

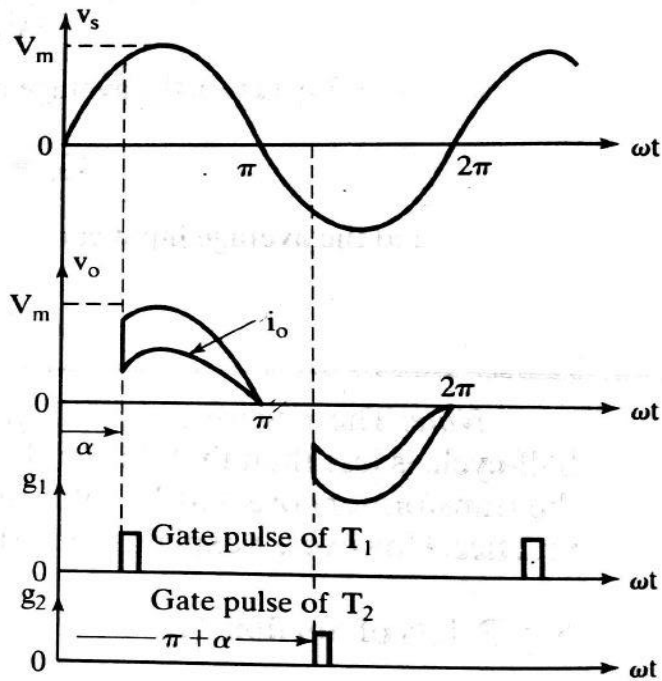

(b) Waveforms

Waveforms for Case II: RL Load

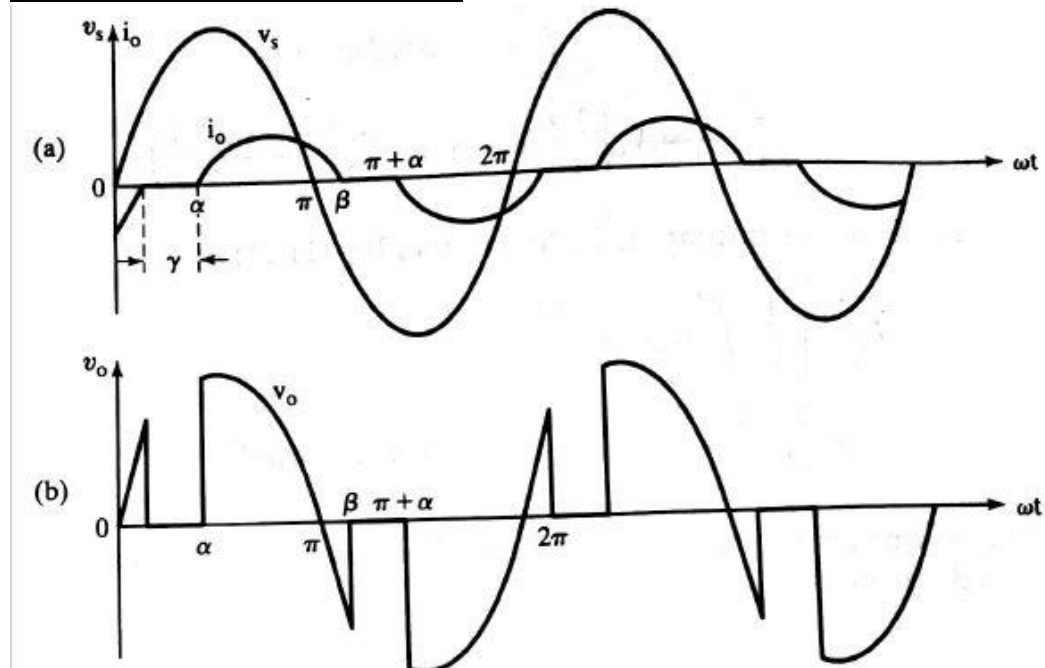




Figure 2 model waveform

1 a) Simulation of Single Phase, Phase controlled Bidirectional AC to AC controller with R load.

Aim: To simulate Single Phase, Phase controlled Bidirectional AC to AC controller with R load in MATLAB Simulink

PROBLEM 1:

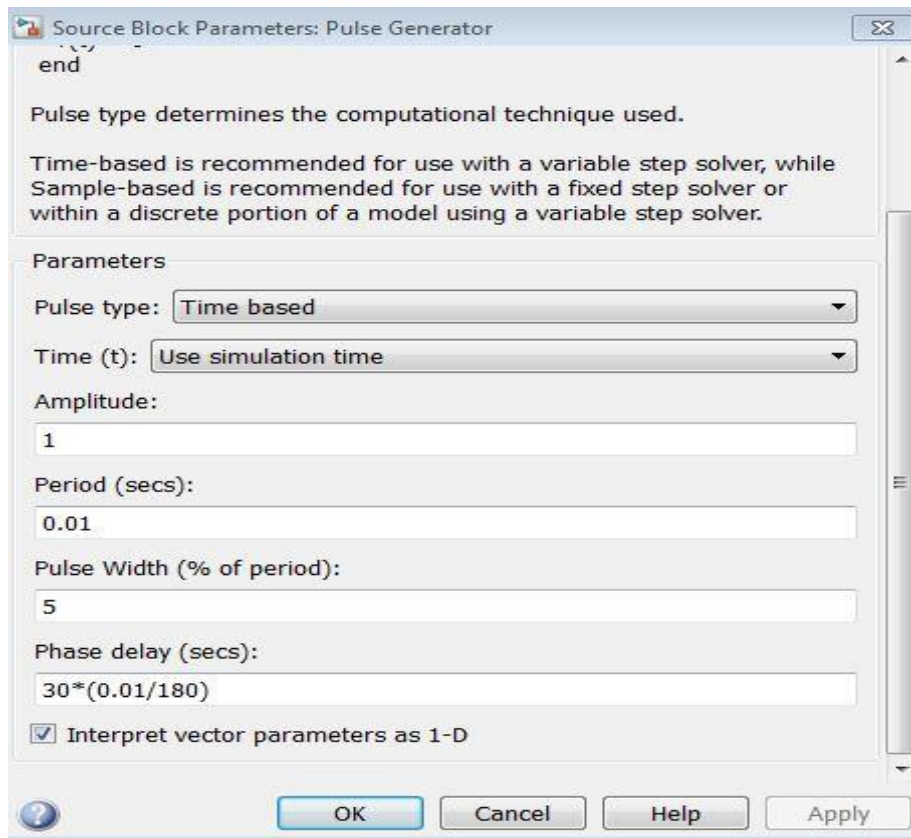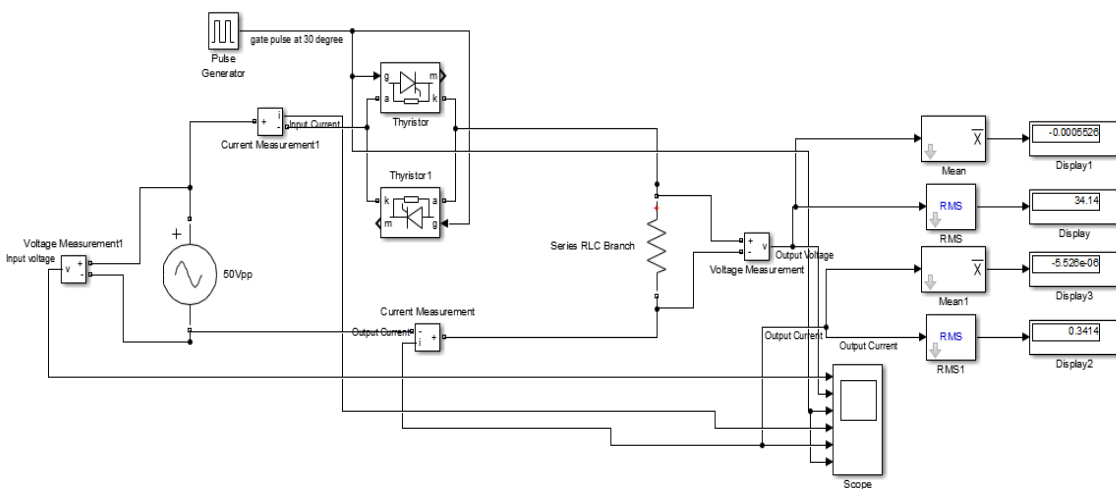a. Implement the 1-phase, Phase controlled Bidirectional AC to AC controller with R load of 12.5Ω and observe the changes in the output voltage waveform at different firing angles. (Input voltage: 50V Peak = **35.35 V (RMS)** and 50Hz)





1 b) Simulation of Single Phase, Phase controlled Bidirectional AC to AC controller with RL load.

Aim: To simulate Single Phase, Phase controlled Bidirectional AC to AC controller with RL load in MATLAB Simulink

PROBLEM 2:

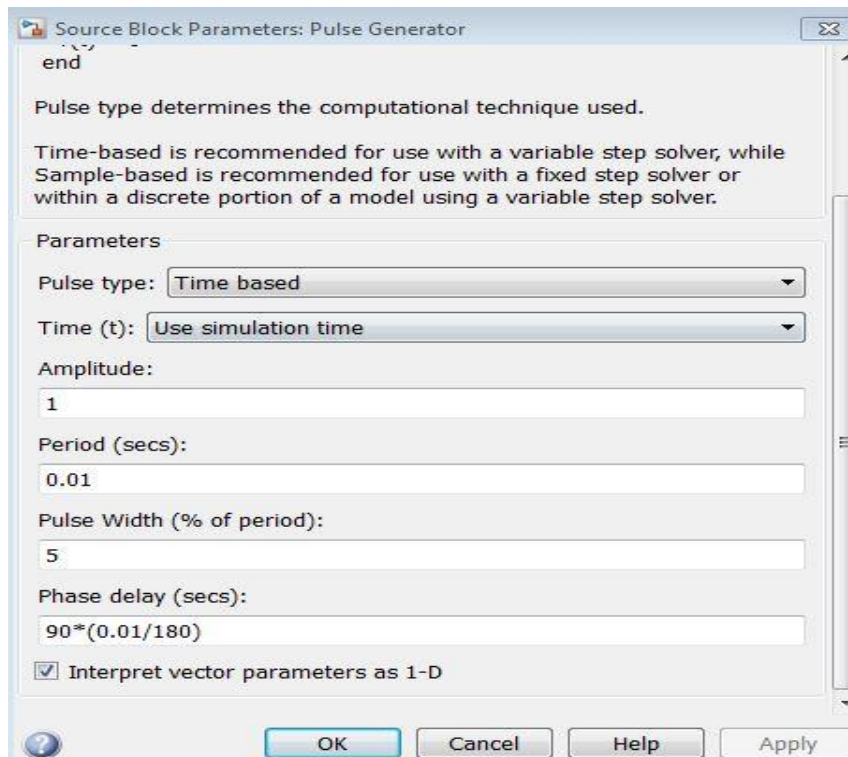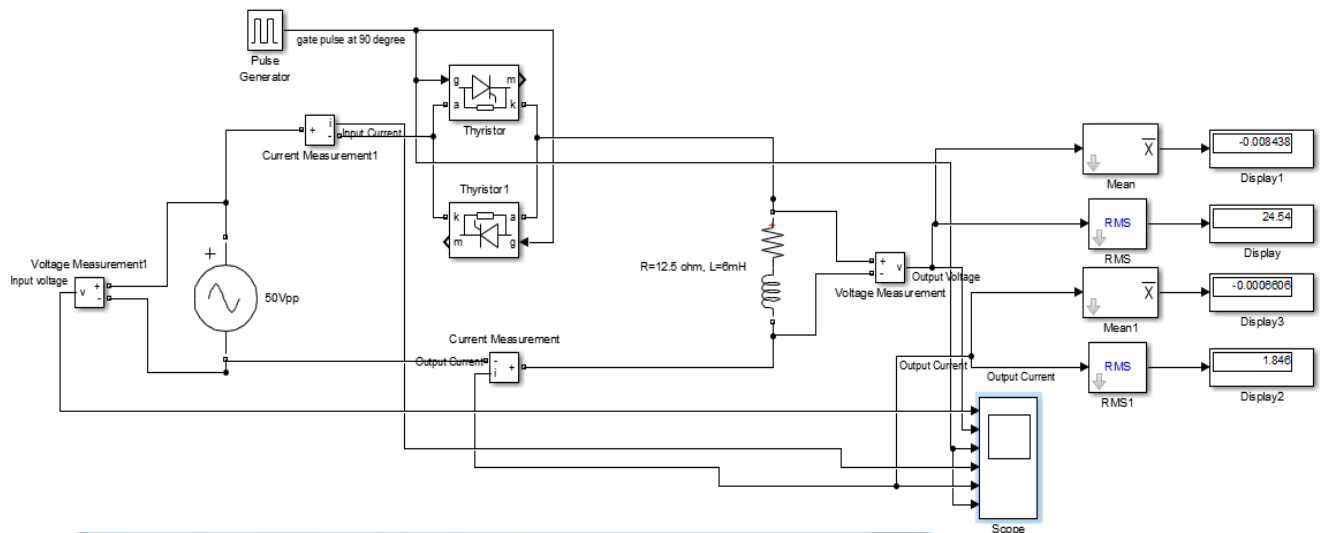- a. Implement the 1-phase, Phase controlled Bidirectional AC to AC controller with the R load of 12.5Ω and L of 6mH and observe the changes in the output voltage waveform at different firing angles. (Input voltage: $50\text{V Peak} = 35.35\text{V (RMS)}$ and 50Hz)



1c). Hardware Implementation Single Phase, Phase controlled Bidirectional AC to AC controller with R Load

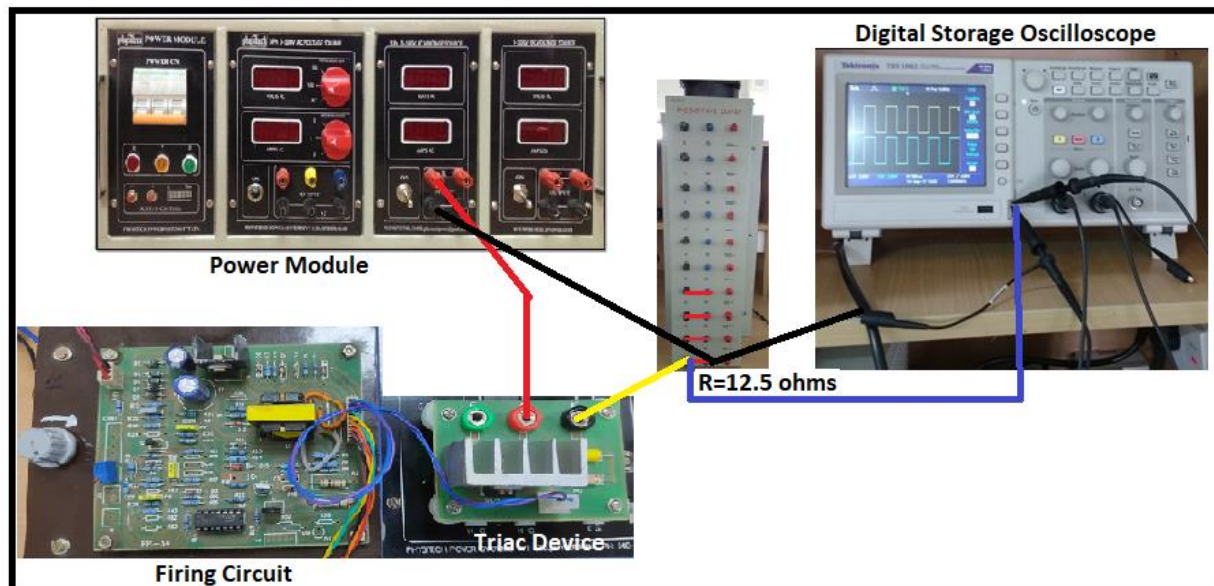


Fig. 3

Procedure:

1. Connect the circuit as shown in the Fig.3. (with R load ($R=12.5 \text{ ohms}$))
2. Switch ON the MCB of 3 ϕ supply on the Left hand side of your Experimental Table.
3. Switch ON the MCB on the POWER MODULE kit.
4. Switch ON the MCB on the SCR-Diode Power module and slowly increase the Voltage to reach up to 35.35 V in RMS using + symbol Push Button in the Power Module kit.

Note: The Voltage Adjustment Controls are a pair of push buttons to finely adjust the voltage to required value.

5. Switch on the driver power switch
6. Connect CRO probes across the R load to measure the output voltage
7. Vary the firing angle as mentioned in the “Exp5_Part B.doc” file.
8. Observe the Output voltage waveforms in the DSO.

1d). Hardware Implementation Single Phase, Phase controlled Bidirectional AC to AC controller with RL Load

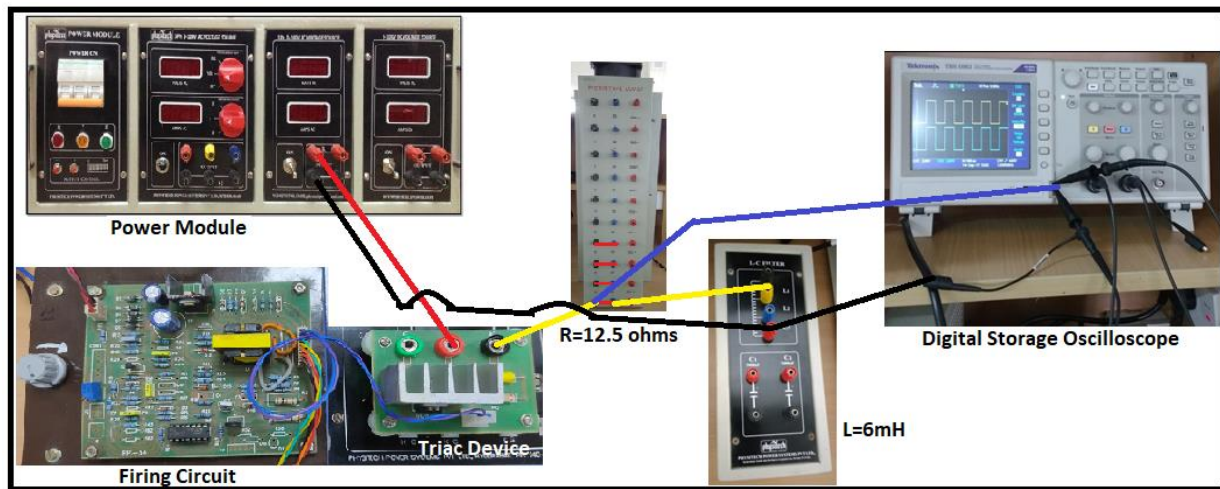


Fig. 4

Procedure:

1. Connect the circuit as shown in the Fig.4 (with RL load ($R=12.5\text{ ohms}$, $L = 6\text{mH}$))
2. Switch ON the MCB of 3 ϕ supply on the Left hand side of your Experimental Table.
3. Switch ON the MCB on the POWER MODULE kit.
4. Switch ON the MCB on the SCR-Diode Power module and slowly increase the Voltage to reach up to 35.35 V in RMS using + symbol Push Button in the Power Module kit.

Note: The Voltage Adjustment Controls are a pair of push buttons to finely adjust the voltage to required value.

5. Switch on the driver power switch
6. Connect CRO probes across the R load to measure the output voltage
7. Vary the firing angle as mentioned in the “Exp5_Part B.doc” file.
8. Observe the Output voltage waveforms in the DSO.

Conclusion: Obtain the results as per “Exp9_Part B.doc” file.